



Lecture 5

Electrical Design


Inductance & Capacitance

February 4, 2025

Reminders and Announcements

- Office hours: Wednesday, 3:30pm-4:30pm
- Homework #1 due Monday, Feb. 10th, by 11:59pm (midnight)
 - Reminder: No late assignments will be accepted unless they are approved by the instructor prior to the deadline
- Download and install ANSYS Electronics Desktop and LTspice and check that you can open them by Thursday
- On Thursday, we will do an in-class ANSYS Q3D tutorial
 - Bring your laptops with the software installed to class

Example: Capacitor Mounted to PCB

 

L_p = partial inductance
 M = mutual inductance of parallel components


$$\begin{aligned}
 L_{total} = & L_{p_{trace1}} + L_{p_{pad1}} + L_{p_{cap}} + L_{p_{pad2}} + L_{p_{trace2}} + L_{p_{via2}} \\
 & + L_{p_{plane}} + L_{p_{via1}} - 2M_{via-via} - 2M_{plane-trace}
 \end{aligned}$$

Effective Inductances for Different Structures

*Note: Tummala textbook 2nd Ed. shows 4π in the denominator, which is incorrect.


• Wire above a ground plane

 - $L_{eff} = \frac{\mu l}{2\pi^*} \cosh^{-1} \left(\frac{2s}{d} \right)$, where l = length, d = diameter, s = spacing
- Package examples: TAB, QFP w/ ground plane
- Typical inductance range: 1 – 10 nH
- Assumes $s \ll l$, and $d \ll s$




• Parallel planes

 - $L_{eff} = \frac{\mu l s}{w}$, where l = length, w = width, s = spacing
- Package examples: PGA, BGA
- Typical inductance range: 0.25 – 1 nH
- Assumes $s \ll l$




Example: Parallel Planes

 

A multi-layer ball grid array (BGA) package has plane layers used to supply both the V_{dd} and the ground (GND). Find the effective inductance for a pair of planes with dimensions of 1 cm by 1 cm, and a spacing of 6 mils.

 
- $L_{eff} = \frac{\mu l s}{w}$, where $l = w = 1 \text{ cm} = 0.01 \text{ m}$, $s = 6 \text{ mils} = 1.5\text{e-}4 \text{ m}$
- $\mu = \mu_0 \mu_r \approx 4\pi \times 10^{-7} \text{ H/m} = 1.26\text{e-}6 \text{ H/m}$
- $L_{eff} = (1.26\text{e-}6 \text{ H/m})(1.5\text{e-}4 \text{ m}) = \mathbf{0.19 \text{ nH}}$



$$V = L \, dI/dt$$

Summary: Inductance

 
- Inductive delay: $\tau = L/R$
- Self inductance: L_p
 - Example: L_{p1} , L_{p2} , L_{p3} , L_{p4}
- Mutual inductance: M
 - Example: $-M_{p1-3}$, $-M_{p2-4}$
 - Subtractive: current flowing in opposite directions (this example)
- Loop inductance: L_{total}
- Example: $L_{total} = L_{p1} + L_{p2} + L_{p3} + L_{p4} - 2M_{p1-3} - 2M_{p2-4}$



$$V = L \, dI/dt$$

Summary: Inductance

 - Example 2: Additive
 - Two parallel wires with current in the same direction
 - Self inductance: L_{p1} , L_{p2}
 - Mutual inductance: M
 - Positive
 - If $s \ll l$: $M = \frac{\mu l}{2\pi} \left[\ln \left(\frac{2l}{s} \right) - 1 \right]$
 - Total inductance if $L_{p1} = L_{p2}$:
 - $L_{parallel} = (L_p + M) / 2$




References on Inductances

- F. W. Grover, “Inductance calculations: working formulas and tables,” https://nvlpubs.nist.gov/nistpubs/bulletin/08/nbsbulletinv8n1p1_A2b.pdf
- Xiaoning Qi, “High frequency characterization and modeling of on-chip interconnects and RF IC wire bonds,” <http://www-tcad.stanford.edu/tcad/pubs/theses/qi.pdf>
- Clayton R. Paul, “Partial and internal inductance,” <https://ieeexplore.ieee.org/document/6507331>
- Eric Bogatin, “Roadmaps of packaging technology,” Chapter 7: Electrical Performance, ISBN: 1-877750-61-1, 1997.

Skin and Proximity Effects


- Skin effect reduces the *internal* wire inductance at high frequencies
- Internal inductance is due to the internal magnetic flux of a conductor
- Internal inductance is typically much less than the external inductance, which is due to external magnetic flux
- Proximity effect reduces the wire inductance by redistributing the currents to form a smaller current loop
- The skin and proximity effect eddy currents superimpose to form the total eddy current distribution

 Internal Inductance vs. Skin Depth/Radius



 
Example: Inductive Delay

- Assume a 5 V supply is feeding a 50 Ω load. The source and return paths between the supply and the load each have 5 nH parasitic inductance. What is the time constant caused by the parasitic inductance?
- $V_{dd} = 5 \text{ V}$, $R = 50 \text{ } \Omega$, $L_1 = L_2 = 5 \text{ nH}$
- $L_{total} = 5 \text{ nH} + 5 \text{ nH} = 10 \text{ nH}$
- $\tau = L_{total}/R = 10 \text{ nH} / 50 \text{ } \Omega = \mathbf{0.2 \text{ ns}}$
- It will take 0.2 ns for the load voltage to reach 3.2 V (63 % of the applied voltage)



 Example: Inductive Delay

- Assume that the source and return paths are close enough such there is 2 nH of mutual inductance between them.
- $V_{dd} = 5 \text{ V}$, $R = 50 \text{ } \Omega$, $L_1 = L_2 = 5 \text{ nH}$, **$M = 2 \text{ nH}$**
- $L_{total} = (2)(5 \text{ nH}) - (2)(2 \text{ nH}) = 6 \text{ nH}$
- $\tau = L_{total}/R = 6 \text{ nH} / 50 \text{ } \Omega = \mathbf{0.1 \text{ ns}}$
- Subtractive M reduces L_{eff} and τ



dI/dt or ΔI Noise

- Transient currents (through interconnects, leads, traces) cause voltage fluctuations on power supply rails due to parasitic inductances
- This is *simultaneous switching noise (SSN)* or dI/dt noise or ΔI noise
- Required charge to energize load to supply voltage V_{dd} : $Q = C \cdot V_{dd}$
- Current draw: $\Delta I = C \cdot V_{dd} / \Delta t$
- If there are N gates switching simultaneously, the current draw from the power supply becomes $\Delta I = N \cdot C \cdot V_{dd} / \Delta t$
- $\Delta V = L \left(\frac{dI}{dt} \right) \rightarrow \Delta I = \Delta V \cdot \Delta t / L_{max}$
- Maximum acceptable inductance: $L_{max} = \Delta t^2 \cdot \Delta V / (N \cdot C \cdot V_{dd})$


Example: dI/dt Noise

- A power supply is supplying 5 CMOS chips with 1 pF load each and a switching time of 1 ns. What is the maximum allowable parasitic inductance L_{max} between the power supply and the chips to achieve a variation in the power supply voltage V_{dd} of $\leq 1\%$?

- $$L_{max} \leq \Delta t^2 \Delta V / N C V_{dd}$$
- $$L_{max} \leq (1 \text{ ns})^2 (0.01)(V_{dd}) / ((5)(0.001 \text{ nF})V_{dd}) = \mathbf{2 \text{ nH}}$$


What if the chip is a single power device with load of 1 nF and 10 ns switching, and $\leq 10\%$ V_{dd} variation is acceptable?

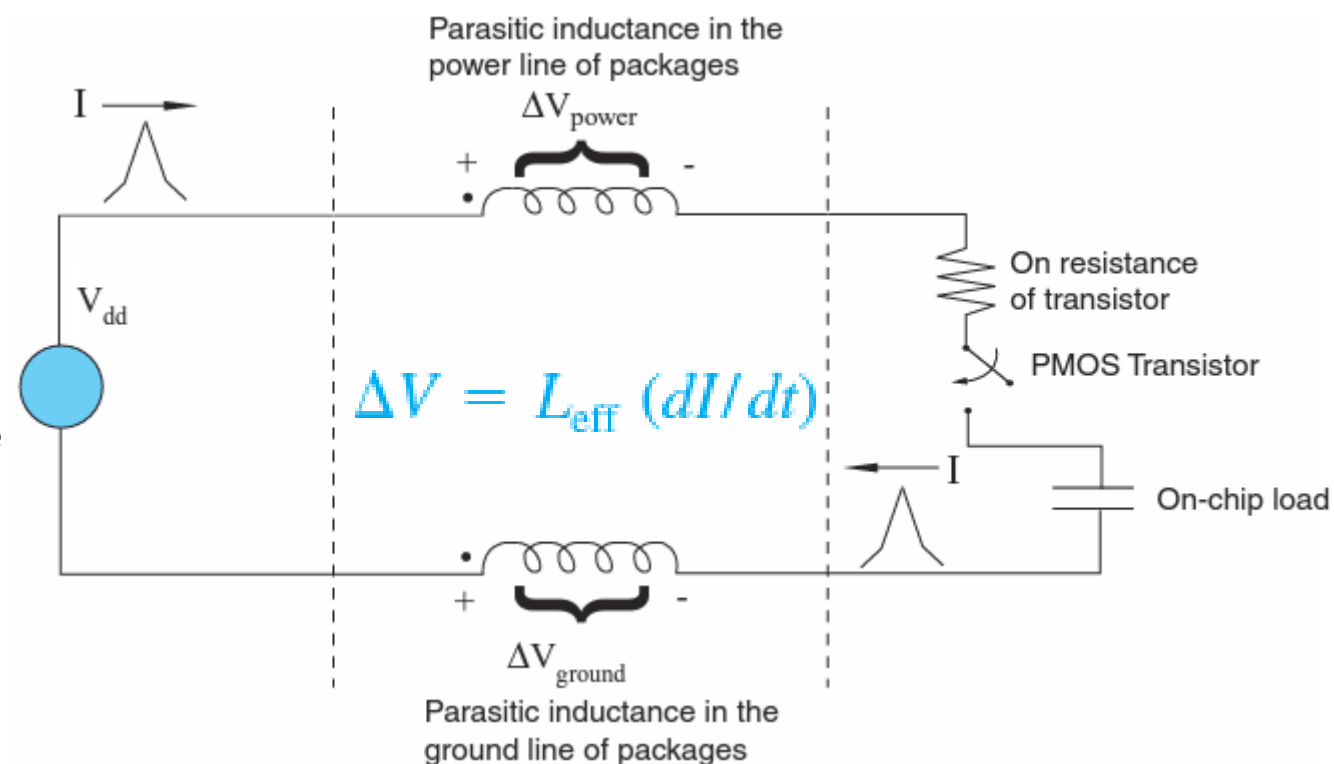- $$L_{max} \leq (10 \text{ ns})^2 (0.1)(V_{dd}) / ((1 \text{ nF})V_{dd}) = \mathbf{10 \text{ nH}}$$




Decoupling Capacitors

On Chip

 

On Package

 

Example: $L_{eff} = 10 \text{ pH}$, 1000 circuits draw 10 A in 0.25 ns.

Find the noise voltage.

- $\Delta V = 400 \text{ mV}$ $\Delta V = L_{eff} (dI/dt)$

Design C_{pkg} to reduce the noise voltage to 200 mV. $C = \Delta I \Delta t / \Delta V$

- $C_{pkg} = 12.5 \text{ nF}$


If $L_{eff} = 5 \text{ pH}$, find the frequency above which C_{pkg} loses effectiveness.

- $f_{max} = 637 \text{ MHz}$

$f_{max} = \frac{1}{2\pi\sqrt{2L_{pkg}C_{pkg}}}$

Limitation of Decoupling Capacitors


More realistic capacitor model:

 


ESR = equivalent series R

ESL = equivalent series L

f_{SR} = self-resonant frequency


 


Package Parasitics




 


Effects of Parasitic Capacitance

  
- Delays
- Oscillations
- Ground currents
- Crosstalk



Capacitive Delay

    


Capacitive Delay

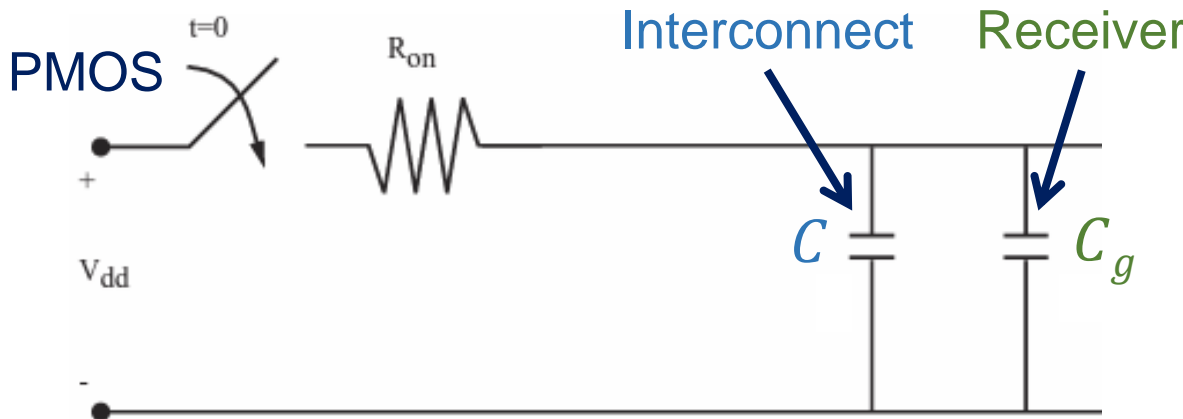

$$V_{load}(t) = V_{dd}[1 - e^{-t/\tau}]$$

$$\tau = R_{on}(C + C_g)$$

 


Example: Capacitive Delay

- $V_{dd} = 5 \text{ V}$; $R_{on} = 50 \text{ } \Omega$; $C + C_g = 10 \text{ pF}$
- $\tau = RC_{total} = (50 \text{ } \Omega)(10 \text{ pF}) = \mathbf{0.5 \text{ ns}}$


How long will it take for V_{load} to rise to 50 % of V_{supply} ?

 - $V_{load}(t) = V_{dd}[1 - e^{-t/\tau}]$
- $-\ln(1 - (0.5)(5 \text{ V})/5 \text{ V}) = 0.69$
- $t_{50\%} = 0.69\tau = \mathbf{0.35 \text{ ns}}$
- $t_{90\%} = 2.3\tau = \mathbf{1.15 \text{ ns}}$



Capacitance (Overlapping Conductors)

 - $Q = CV$
- Taking derivative:
 - $I = dQ/dt$
 - $I = C dV/dt$
- $C = \epsilon A/d$
 - ϵ = permittivity
 - $\epsilon = \epsilon_r \epsilon_0$
 - $\epsilon_0 = 8.86 \times 10^{-12}$ F/m, permittivity of free space
 - ϵ_r = relative permittivity or dielectric constant (material property)
 - A = overlapping area
 - d = distance



Example: Capacitance (Overlapping Conductors)

- Al_2O_3 substrate (e.g., DBC): $\epsilon_r = 9.4$
- FR4 substrate (e.g., PCB): $\epsilon_r = 4.4$

- $C = \epsilon A / d = \epsilon_0 \epsilon_r A / d$

- $\epsilon_0 = 8.86 \times 10^{-12} \text{ F/m}$


- $A = 10 \text{ mm} \times 4 \text{ mm} = 40 \text{ mm}^2$

- $C = (8.86 \times 10^{-12} \text{ F/m})(\epsilon_r)(4 \times 10^{-5} \text{ m}^2) / (0.0005 \text{ m})$

- $C_{\text{Al}_2\text{O}_3} = 6.7 \text{ pF}$ (Q3D: 7.7 pF)


- $C_{\text{FR4}} = 3.12 \text{ pF}$ (Q3D: 3.7 pF)

 ➤ Substrate materials with higher relative permittivity (dielectric constant) have higher parasitic capacitance



 Example: Capacitance (Adjacent Conductors)

- Formula for adjacent conductors with equal widths:
- $C' = 0.122 t/s + 0.0905 (1 + \epsilon_r) a$ [pF/cm]
- $a = \log (1 + 2 w/s + 2 \sqrt{w/s} + w^2 / 200)$
- s = distance between two adjacent conductors, mm
- t = thickness, mm
- w = conductor width, mm
- ϵ = permittivity
- $C = C' l$
- l = parallel running length, cm



Example: Capacitance (Adjacent Conductors)

- $C' = 0.122 \, t/s + 0.0905 (1 + \epsilon_r) a$ [pF/cm]
- $a = \log (1 + 2 \, w/s + 2 \sqrt{w/s} + w^2 / 200)$
- $C = C' l$

Find the capacitance between the adjacent traces.


Al_2O_3 substrate (e.g., DBC): $\epsilon_r = 9.4$

$$C' = 1.1 \, \text{pF/cm}$$

$$C = 2.2 \, \text{pF}$$

(Q3D: 1.3 pF for $t_{\text{Al}_2\text{O}_3} = 1 \, \text{mm}$)

 (Q3D: 2.1 pF for $t_{\text{Al}_2\text{O}_3} = 5 \, \text{mm}$)



Coupling Capacity vs Spacing

To decrease C :

- Increase spacing between conductors
- Decrease conductor width
- Choose materials with low dielectric constant
- These will also impact the L , R , and thermal conductivity


 



Fig. 2-4 Capacitive coupling between adjacent conductors

High-Capacitance vs Low-Capacitance Layouts

 - High parasitic capacitance
 - Wide traces
 - Large overlap area
 - Close adjacent traces




 
- Low parasitic capacitance
 - Reduced width
 - Eliminate overlap
 - Increase spacing between adjacent traces



$$I = C dV/dt$$

Summary: Capacitance

- Capacitive delay: $\tau = RC$
- Overlapping conductors:
 - $C = \epsilon A/d$, where A = overlapping area
 - Decrease by decreasing overlapping area, increasing distance d , or using a material with lower dielectric constant ϵ_r
- Adjacent conductors:
 - $C' = 0.122 t/s + 0.0905 (1 + \epsilon_r) a$ [pF/cm]
 - $a = \log (1 + 2 w/s + 2 \sqrt{w/s} + w^2 / 200)$
 - $C = C' l$
 - Decrease by increasing spacing s between conductors, reducing t , w , and l of conductors, or using material with lower ϵ_r

  

Summary: Types

- Resistance
 - DC (temperature dependent)
 - AC (skin and proximity effects)
- Inductance
 - Self/partial inductance
 - Mutual inductance
 - Total/loop/effective inductance
- Capacitance
 - Between overlapping conductors
 - Between adjacent conductors

Summary: Consequences

- Resistance
 - Power loss
 - Heating
 - Ground bounce
- Inductance
 - Delay
 - Noise
 - Oscillation
 - Voltage overshoot
- Capacitance
 - Delay
 - Noise
 - Oscillation

Summary: Mitigation Approaches

- Resistance

- DC – increase conductivity, decrease length, increase area
- AC – increase circumference/perimeter, multiple smaller conductors in parallel

- Capacitance

- Minimize overlapping areas
- Increase spacing between traces/interconnects
- Low dielectric constant

- Inductance

- Reduce loop area
- Decrease conductor length
- Decrease spacing between the source and return paths
- Increase spacing between conductors with same current direction
- Use decoupling capacitors
- Arrange conductors perpendicular to minimize unwanted coupling

Next Class

- Electrical Design (Chapter 2)
 - Intro to Finite Element Analysis (FEA) and ANSYS Q3D
 - Start Q3D in-class tutorial